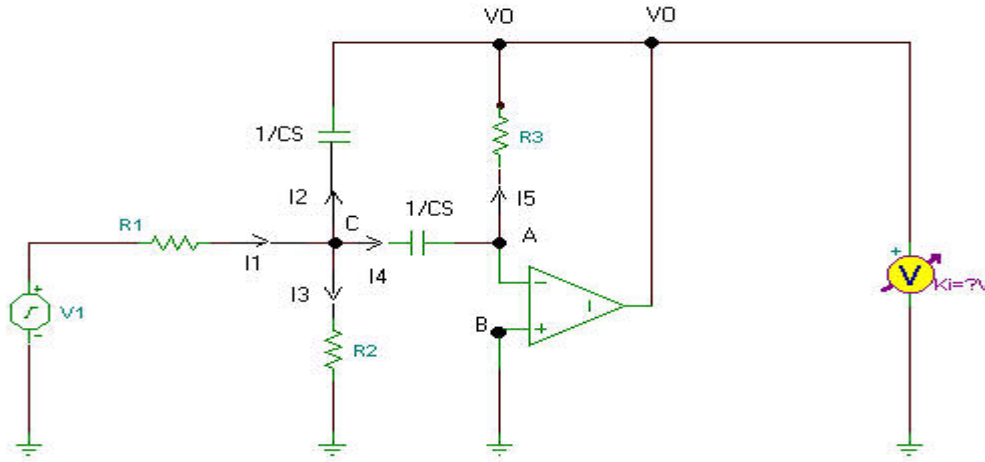


TINA'S STUDENT CONTEST

KELIRIS SOTIRIS SOLUTION: I permit designsoftware to publish my solution on their website.

Using the laplace transform we have the circuit below:



The nodes of the circuit are A,B,C and V_0 .(V_0 is V_{OUT})

The AC transfer function of the circuit is given by the formula $W(s)=V_0/V_1$

From the ideal opamp(operational amplifier) we know that $V_A=V_B$

$$V_B=0 \Rightarrow \underline{V_A=0} \quad (1)$$

If we use Ohm's law in node A we get :

$$I_4=I_5 \Rightarrow \frac{(V_C-V_A)}{(1/CS)} = \frac{(V_A-V_0)}{R_3}$$

But V_A is 0 (relationship (1)) so we get :

$$\frac{V_C}{(1/CS)} = \frac{-V_0}{R_3} \quad (2) \quad \text{and} \quad V_C = \frac{-V_0}{R_3CS} \quad (3)$$

If we use Ohm's law in node C we get :

$$I_1=I_2+I_3+I_4 \Rightarrow \frac{(V_1-V_C)}{R_1} = \frac{(V_C-V_0)}{1/CS} + \frac{V_C}{R_2} + \frac{V_C}{1/CS} \quad (4)$$

Now all we have to in order to find the transfer function is to substitute relationships (2) and (3) into relationship (4)

Thereby $\Rightarrow \frac{V_1}{R_1} + \frac{V_0}{R_1 R_3 C S} = -V_0 C S - \frac{V_0 C S}{R_3 C S} - \frac{V_0 C S}{R_2 R_3 C S} - \frac{V_0 C S}{R_3 C S}$


$$\Rightarrow \frac{V_1}{R_1} = -\frac{V_0}{R_1 R_3 C S} - V_0 C S - \frac{2V_0 C S}{R_3 C S} - \frac{V_0 C S}{R_2 R_3 C S}$$

$$\Rightarrow \frac{V_1}{R_1} = -\frac{(V_0 R_2 + V_0 R_1 + 2V_0 C S R_1 R_2 + V_0 C S R_1 R_2 R_3 C S)}{R_1 R_2 R_3 C S}$$

$$V_1 = -\frac{V_0 (R_2 + R_1 + 2C S R_1 R_2 + V_0 R_1 R_2 R_3 C^2 S^2)}{R_2 R_3 C S} \quad (C^2 S^2 = C * C * S * S)$$

Finally $W(S) = \frac{-R_2 R_3 C S}{(R_1 + R_2 + 2C S R_1 R_2 + R_1 R_2 R_3 C^2 S^2)}$

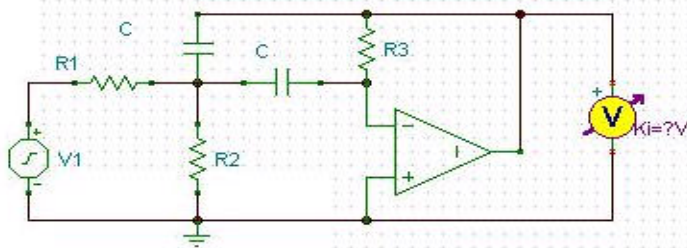and it is the same result as TINA's Analysis/Symbolic Analysis/AC Transfer/ returned to us as shown below.



Επεξεργαστής Εξισώσεων

Αρχείο Επεξεργασία Ρυθμίσεις Βοήθεια

Transfer function:

$$W(s) = \frac{R_2 \cdot C \cdot R_3 \cdot s}{-R_1 - R_2 - 2 \cdot R_2 \cdot R_1 \cdot C \cdot s - R_2 \cdot R_1 \cdot C^2 \cdot R_3 \cdot s^2}$$